

# OXFORD CAMBRIDGE AND RSA EXAMINATIONS Advanced Subsidiary GCE

PHYSICS A 2822

**Electrons and Photons** 

Monday

**12 JANUARY 2004** 

Morning

1 hour

Candidates answer on the question paper. Additional materials: Electronic calculator

Candidate Name	Centre Number	Candidate Number

#### TIME 1 hour

#### **INSTRUCTIONS TO CANDIDATES**

- Write your name in the space above.
- Write your Centre number and Candidate number in the boxes above.
- Answer all the questions.
- Write your answers in the spaces provided on the question paper.
- Read each question carefully and make sure you know what you have to do before starting your answer.

#### **INFORMATION FOR CANDIDATES**

- The number of marks is given in brackets [] at the end of each question or part question.
- You will be awarded marks for the quality of written communication where this is indicated in the question.
- You may use an electronic calculator.
- You are advised to show all the steps in any calculations.

FOR EXAMINER'S USE					
Qu.	Max.	Mark			
1	7				
2	9				
3	6				
4	5				
5	16				
6	17				
TOTAL	60				

#### Data

speed of light in free space,	$c = 3.00 \times 10^8 \mathrm{ms^{-1}}$
permeability of free space,	$\mu_0 = 4\pi \times 10^{-7}  \mathrm{H  m^{-1}}$
permittivity of free space,	$\epsilon_0 = 8.85 \times 10^{-12}  \mathrm{F  m^{-1}}$
elementary charge,	$e = 1.60 \times 10^{-19} \mathrm{C}$
the Planck constant,	$h = 6.63 \times 10^{-34} \mathrm{J}\mathrm{s}$
unified atomic mass constant,	$u = 1.66 \times 10^{-27} \text{ kg}$
rest mass of electron,	$m_{\rm e} = 9.11 \times 10^{-31}  \rm kg$
rest mass of proton,	$m_{\rm p} = 1.67 \times 10^{-27}  \rm kg$
molar gas constant,	$R = 8.31 \text{ J K}^{-1} \text{ mol}^{-1}$
the Avogadro constant,	$N_{\rm A} = 6.02 \times 10^{23}  {\rm mol}^{-1}$
gravitational constant,	$G = 6.67 \times 10^{-11} \text{ N m}^2 \text{ kg}^{-2}$
acceleration of free fall,	$g = 9.81 \text{ m s}^{-2}$

#### Formulae

$$s = ut + \frac{1}{2}at^2$$

$$n = \frac{1}{\sin C}$$

 $v^2 = u^2 + 2as$ 

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

$$C = C_1 + C_2 + \dots$$

$$x = x_0 e^{-t/CR}$$

$$p = \frac{1}{3} \frac{Nm}{V} < c^2 >$$

radioactive decay,

$$X = X_0 e^{-\lambda t}$$

$$t_{\frac{1}{2}} = \frac{0.693}{\lambda}$$

critical density of matter in the Universe,

$$\rho_0 = \frac{3H_0^2}{8\pi G}$$

$$=\sqrt{(1-\frac{v^2}{c^2})}$$

current,

$$I = nAve$$

nuclear radius,

$$r = r_0 A^{1/3}$$

sound intensity level,

$$= 10 \lg \left(\frac{I}{I_0}\right)$$

### Answer all the questions.

1 (	(a)	Exp	lain	what is meant by <i>electric current</i> .
(	(b)	The	:SI ι	unit of electric charge is the coulomb. Define the <i>coulomb</i> .
				[1]
(	(c)	Fig.	1.1	shows two strips of aluminium foil connected to a d.c. supply.
				d.c. supply o- strips of aluminium foil
				Fig. 1.1
		The	swit	tch <b>S</b> is closed.
		(i)	The	e charge flow past a particular point in one of the aluminium strips is 340 C in a e of 50 s. Calculate the current in this aluminium strip.
				A [O]
				current = A [2]
		(ii)	1	There is a force between the two aluminium strips when the switch is closed. State why each of the aluminium strips experiences a force.
			2	Name the rule that may be used to determine the direction of the force on a current-carrying wire in an electric motor.
			3	State the direction of the force experienced by the aluminium strip <b>B</b> .
				[3]
				[Total: 7]

(i) Name the component with the I/V characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component depon the potential difference V across it. You are advised to show any calculations.	Fig. 2.1  // Characteristic shown in Fig. 2.1.  [1]  ailable for the quality of written communication.  g. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component depth o	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1]  ailable for the quality of written communication.  g. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component deposition.	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1]  ailable for the quality of written communication.  g. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component depth o	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1]  ailable for the quality of written communication.  g. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component depth o	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1]  ailable for the quality of written communication.  g. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component deposition.	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1]  ailable for the quality of written communication.  g. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component deposition.	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1]  ailable for the quality of written communication.  g. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component department departmen	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1] ailable for the quality of written communication.  Ig. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component department departmen	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1] ailable for the quality of written communication.  Ig. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component department.	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1] ailable for the quality of written communication.  Ig. 2.1, how the resistance of the component depends
Fig. 2.1  (i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.  (ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component department.	Fig. 2.1  If V characteristic shown in Fig. 2.1.  [1] ailable for the quality of written communication.  If you have a second communication in Fig. 2.1.
<ul> <li>(i) Name the component with the I/V characteristic shown in Fig. 2.1.</li> <li>(ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component dependence.</li> </ul>	//V characteristic shown in Fig. 2.1. [1] ailable for the quality of written communication. g. 2.1, how the resistance of the component depends
<ul> <li>(i) Name the component with the <i>I/V</i> characteristic shown in Fig. 2.1.</li> <li>(ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component dependence.</li> </ul>	//V characteristic shown in Fig. 2.1. [1] ailable for the quality of written communication. g. 2.1, how the resistance of the component depends
(ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component dep	ailable for the quality of written communication.  g. 2.1, how the resistance of the component depends
(ii) In this question, one mark is available for the quality of written communication Describe, making reference to Fig. 2.1, how the resistance of the component dep	ailable for the quality of written communication. g. 2.1, how the resistance of the component depends
Describe, making reference to Fig. 2.1, how the resistance of the component dep	g. 2.1, how the resistance of the component depends
on the potential difference V across it. You are advised to show any calculations.	ss it. You are advised to show any calculations.

[Total: 9]

3	(a)	State Kirchhoff's first law.	

(b) Fig. 3.1 shows part of an electrical circuit.

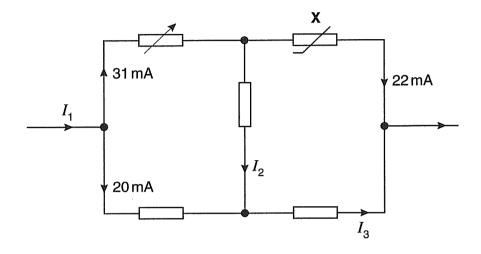


Fig. 3.1

(i) Name the component marked X.

.....[1]

(ii) Determine the magnitude of the currents  $I_{\rm 1}$ ,  $I_{\rm 2}$  and  $I_{\rm 3}$ .

 $I_1$  = ..... mA

 $I_2$  = ..... mA

 $I_3$  = ..... mA

[3]

[Total: 6]

4 Fig. 4.1 shows an electrical circuit.

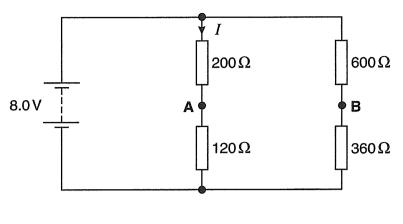


Fig. 4.1

The battery has negligible internal resistance.

(a) Show that the current I is 25 mA.

(b) Calculate the potential difference (p.d.) across the resistor of resistance  $120\,\Omega$ .

(c) Explain why a voltmeter connected between points A and B will read 0 V.

······································
[C]

[Total: 5]

[2]

5 Fig. 5.1 shows a plan view of an electrical circuit that includes a flat circular coil.

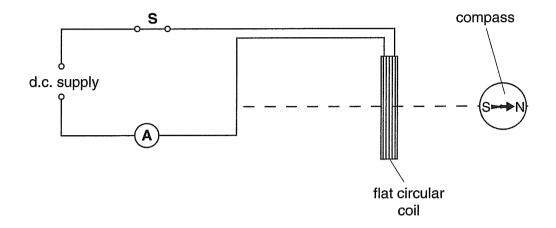


Fig. 5.1

(a) A small compass is placed close to the coil along its axis. When the switch **S** is closed, the compass needle deflects so that it points in the direction shown in Fig. 5.1.

On Fig. 5.1, draw the magnetic field pattern for the flat circular coil. [2]

- (b) The coil is made from insulated wire of cross-sectional area 8.4 x  $10^{-7}$  m<sup>2</sup>. At room temperature, the material of the wire has resistivity 4.9 x  $10^{-7}\Omega$  m. The coil consists of 20 turns and has a mean radius 2.8 cm.
  - (i) Show that the total length of the wire is 3.5 m.

[1]

(ii) Calculate the resistance of the coil.

resistance = .....  $\Omega$  [3]

(c) Fig. 5.2 shows the variation with time t of the current I in the circuit after the switch S has been closed.

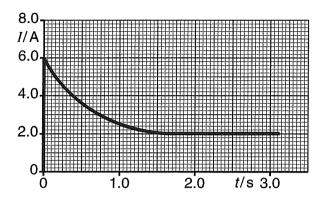


Fig. 5.2

(i)	Calculate	the	potential	difference	(p.d.)	across	the	coil	immediately	after	the
	switch S is	clo	sed.						-		

(ii) Calculate the power dissipated by the coil immediately after the switch **S** is closed.

	power = unit [3]
(iii)	In this question, one mark is available for the quality of written communication.
	Explain why the current changes as shown in Fig. 5.2.
	, ·

Quality of Written Communication [1]

[Total: 16]

(a)	State what property of electromagnetic radiation is demonstrated by the photoelectric effect.
	[1]
(b)	Define each of the following terms
	(i) photon
	[1]
	(ii) threshold frequency.
	[1]
(2)	
(c)	An argon-laser emits electromagnetic radiation of wavelength $5.1 \times 10^{-7}$ m. The radiation is directed onto the surface of a caesium plate. The work function energy for caesium is $1.9  \text{eV}$ .
	(i) Name the region of the electromagnetic radiation emitted by the laser.
	[1]
	(ii) Show that the work function energy of caesium is $3.0 \times 10^{-19} J$ .
	[1]
	(iii) Calculate
	1 the energy of a single photon
	energy = J [2]
	2 the maximum kinetic energy of an electron emitted from the surface of caesium.
	Linatia anavar
	kinetic energy = J [3]

	an emitted electron if the intensity of the laser light is reduced.	of of
		••••
		[2]
	(v) The power of the laser beam is 80 mW. Calculate the number of electrons emit per second from the caesium plate assuming that only 7.0% of the incid photons interact with the surface electrons.	
	number = s <sup>-1</sup>	[2]
(d)	Moving electrons have a wave-like property. Calculate the speed $\nu$ of an elect having a de Broglie wavelength equal to the wavelength of the laser light in (c).	ron
	$v = \dots m s^{-1}$	[3]
	[Total:	
	1	,

**END OF QUESTION PAPER** 

OCR has made every effort to trace the copyright holders of items used in this Question paper, but if we have inadvertently overlooked any, we apologise.

## 2822: Electrons and photons

1		
(a)	Flow / movement of charge / charged particle(s)  (Allow current = rate of flow of charge / current = rate of charge of charge)  AW	B1
(b)	The charge (flowing past a point) in 1s when current is 1 A (Allow $1C = 1A \times 1s$ )	B1
(c)(i)	$I = \frac{\Delta Q}{\Delta t}$ / $I = \frac{340}{50}$ (Allow any subject - with or without $\Delta$ )	C1
	6.8 (A)	<b>A</b> 1
(c)(ii)1	There is magnetic field (around the current-carrying strip(s) and hence a force) AW	B1
2	2. (Fleming's) left-hand rule	B1
3	3. Towards A / To the left (Allow direction given on Fig.1.1)	B1 [ <b>Total : 7</b> ]
2		
(a)	current $\infty$ voltage / p.d. (for a metal conductor) [Allow $I \propto V$ because of <b>(b)</b> ] as long as temperature remains constant / all physical conditions remain the same	M1 A1
	( $V = IR$ and $R = \text{constant}$ scores 1/2) ( $V = IR$ scores 0/2)	
(b)(i)	(Semiconductor) diode	B1
(b)(ii)	Any five from:	B1 × 5
	Resistance is given by $R = V/I$ (Allow the use of R for resistance in this question) The resistance is not constant / Diode is a non-ohmic (component)	
	For $\underline{\text{negative}}$ value(s) (of $V$ ) resistance is infinite / (very) large (Allow a calculation)	r e
	For $V$ / value(s) less than 0.6 (V) the resistance is infinite / (very) large (Accept 0.62 V) For $V$ / value(s) greater than 0.6 (V) the resistance is small / less	
	For $V$ / value(s) greater than 0.6 (V) the resistance decreases (as $V$ increases) (Also scores mar	
	Resistance correctly calculated at one point (Assume values are in ohms if unit is not give Resistance correctly calculated at another point	en)
	(Allow 'voltage increases the resistance decreases' if there is no reference to 0.6 V and the sec above is not scored)	cond mark
		<b>B</b> 1
	QWC 'Spelling and grammar'	[Total : 9]
•		
3 (a)	sum of current(s) into a point / junction = sum of current(s) out (from the point / junction) (-1 for omission of 'point' or 'sum' in the statement of the law) (Algebraic sum of current(s) at a point = 0 scores 2/2)	B2
		D1
(b)(i)	Thermistor	B1
(b)(ii)		B1
	$I_2 = 9 \text{ (mA)}$ $I_3 = 29 \text{ (mA)}$	B1 B1
	-3 ( /	[Total : 6]

January 2004 2822 **Final Mark Scheme** 4 C1  $R = R_1 + R_2 / R = 200 + 120 / R = 320$ (a) current =  $\frac{8.0}{320}$ C1 current =  $2.5 \times 10^{-2}$  (A) A<sub>0</sub>  $V = 25 \times 10^{-3} \times 120$   $V = \frac{120}{120 + 200} \times 8.0$ (b) **B**1 V = 3.0 (V)p.d. across the 360 ( $\Omega$ ) resistor = p.d. across the 120 ( $\Omega$ ) resistor / (c) **B**1 There is no current between A and B / in the voltmeter (Allow 'A & B have same voltage' - BOD) The p.d. calculated across 360  $\Omega$  resistor is shown to be 3.0 V / The ratio of the resistances of the resistors is shown to be the same. B1 [Total : 5] 5 **B**1 Correct field direction (a) **B**1 Correct field pattern (minimum of three lines)  $length = 2\pi \times 2.8 \times 10^{-2} \times 20$ M1 length =  $2\pi \times 2.8 \times 20$ (b)(i) A<sub>0</sub> length =  $3.52 (m) \approx 3.5 (m)$ length  $\approx 350$  (cm) C1 (Allow any subject)

(b)(ii)  $R = \frac{\rho L}{A}$  (Allow any subject) C1  $R = \frac{4.9 \times 10^{-7} \times 3.5}{8.4 \times 10^{-7}}$   $R = 2.04 \approx 2.0 \,(\Omega)$  ( $R = 2.05 \approx 2.1 \,\Omega$  if 3.52 m is used) A1

(c)(i)  $V = 6.0 \times 2.04$  (Possible ecf) (Allow initial current 5.7 A to 6.0 A) C1  $V = 12.2 \approx 12$  (V) (Allow  $V = 2.0 \times 2.04 \approx 4.1$  (V) 1 mark) A1

(c)(ii) P = VI (Allow  $P = I^2R$  or  $P = V^2/R$ ) C1  $P = 12 \times 6.0$  (Possible ecf) P = 72 A1 watt / W / J s<sup>-1</sup> / VA

(c)(iii) Any <u>four</u> from:

The temperature of the coil increases / the coil gets 'hotter' (Allow 'coil heats up')

The resistance / resistivity of coil increases (as its temperature increases)

The decrease in current is linked to I = V/R

QWC 'Organisation'

More / frequent collisions of electrons and (vibrating) atoms / ions (as temperature / resistance increases)
The coil (eventually) reaches steady temperature / constant (higher) resistance

The coil (eventually) reaches steady temperature / constant (figher) resistance

B1 [**Total : 16**]

 $B1 \times 4$ 

6

- (a) particle(-like) / particulate (nature) / photon ('behaviour')

  B1
- (b)(i) A 'packet' of energy / radiation / A quantum of (EM) radiation / energy / light B1 (Do not allow 'particle of light')
- (b)(ii) The minimum frequency (of the EM radiation) for emission of electrons / photoelectric effect

  B1
- (c)(i) Visible (light)
- (c)(ii) work function =  $1.9 \times 1.6 \times 10^{-19}$  M1 work function =  $3.04 \times 10^{-19}$  (J)  $\approx 3.0 \times 10^{-19}$  (J)
- (c)(iii)1. $E = hf / E = \frac{hc}{\lambda}$   $6.63 \times 10^{-34} \times 3.0 \times 10^{8}$

$$E = \frac{6.63 \times 10^{-34} \times 3.0 \times 10^{8}}{5.1 \times 10^{-7}}$$

$$E = 3.9 \times 10^{-19} \text{ (J)}$$
A1

2. 
$$hf = \phi + KE_{(max)}$$
 /  $hf = \phi + \frac{1}{2} mv^2$  (Allow  $E = \phi + \frac{1}{2} mv^2$  if  $E$  is qualified in (c)(iii)1.) C1  
3.9 × 10<sup>-19</sup> = 3.0 × 10<sup>-19</sup> + KE<sub>(max)</sub> / 3.9 × 10<sup>-19</sup> = 3.04 × 10<sup>-19</sup> + KE<sub>(max)</sub> C1  
KE = 9.0 × 10<sup>-20</sup> (J) / KE = 8.6 × 10<sup>-20</sup> (J) (Possible ecf) A1

- (c)(iv) No change (to maximum KE of electron)

  Each photon has same energy (but there are fewer photons)

  B1
- (c)(v) number of photons =  $\frac{80 \times 10^{-3}}{3.9 \times 10^{-19}}$  ( $\approx 2.05 \times 10^{17}$ ) (Possible ecf)

number of electrons =  $0.07 \times \frac{80 \times 10^{-3}}{3.9 \times 10^{-19}}$ number of electrons =  $1.44 \times 10^{16} (s^{-1}) \approx 1.4 \times 10^{16} (s^{-1})$  A1

(d) 
$$\lambda = \frac{h}{mv}$$
 (Allow any subject)

$$5.1 \times 10^{-7} = \frac{6.63 \times 10^{-34}}{9.11 \times 10^{-31} \times v}$$

$$v = 1.43 \times 10^{3} \approx 1.4 \times 10^{3} \text{ (ms}^{-1)}$$
A1

[Total: 17]

January 2004